

Plotted:

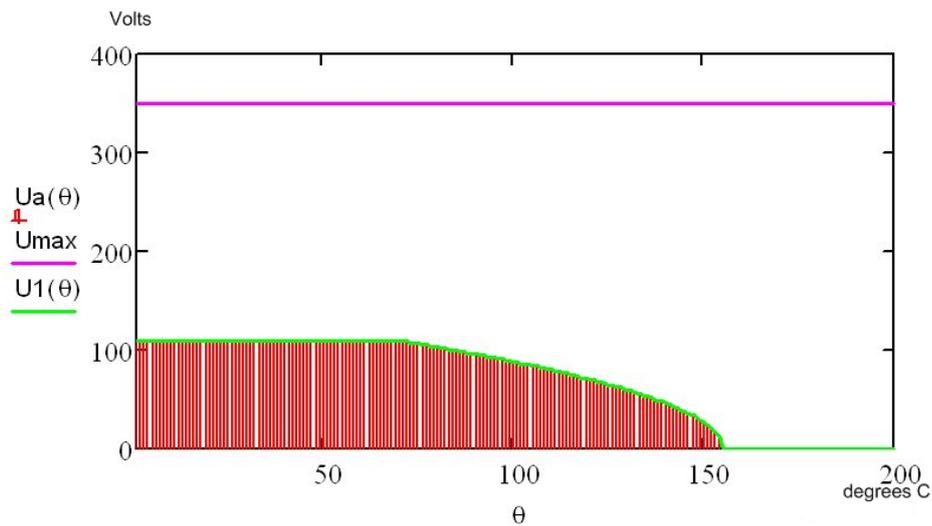


Fig.2 Plot of the admissible voltage

- $U_{max}(\theta) = 350 \text{ V}$ constant (straight line),
- $U_1(\theta) = \sqrt{P_d(\theta) \cdot R_n}$
- $U_a(\theta) = \min(U_{max}, U_1(\theta))$ (hashed area).

The maximum appliable voltage is plotted for different values of the ambient temperature:

- $U_a(1)$ U_a at 1 °C,
- $U_a(\theta_n)$ U_a at the rated temperature,
- $U_a(\theta_1)$ U_a for a temperature between the rated and maximum temperature,
- $U_a(\theta_{max})$ U_a at the maximum temperature.

Obs.: $U_a(\theta_{max}) = 0$ (always)

The range for the applied voltages onto a resistor depends on its critical resistance:

$$R_{crt} = U_{max}^2 / P_n$$

It results $R_{crt} = 245 \text{ k}\Omega$ for the parameters given above.

- Three values of the rated resistance R_n have to be chosen, such that $R_n \approx \square R_{crt} / 10$, $R_n = R_{crt}$, $R_n \approx R_{crt} \times 10$. For the three values, establish the correlation with the aspects mentioned in the previous sections, the range of applied voltages for each resistor. Plot the graphs and mention on the axis the corresponding values for the temperatures and voltages and comment upon the results.
- Discuss the three cases of the rated resistance for the values of the voltage $U_a(\theta)$ at 20 degrees, at the rated temperature and at θ_1 .

2. The analysis of the stress for a group of resistors:

2.1 Graphical resolution for the stress problem for a group of resistors

After passing item 1 determine the maximum voltage which can be applied at the terminals of a

parallel grouping of resistors. The circuit is working in an unstable environment with respect to temperature. The temperature interval is θ_a (10..155) degrees C. The types and parameters of the resistors are:


- a) A carbon film resistor TA670, manufacturer Multicomp
 - $R_{n1} = 47 \text{ K}\Omega$ rated resistance,
 - $P_{n1} = 0.25 \text{ W}$ rated power
 - $U_{max1} = 250 \text{ V}$ maximum voltage
 - $\theta_{n1} = 70^\circ\text{C}$ rated temperature
 - $\theta_{max1} = 155^\circ\text{C}$ maximum temperature

- b) A carbon composition resistor CBT50, manufacturer Tyco Electronics
 - $R_{n2} = 500000 \Omega$ rated resistance,
 - $P_{n2} = 0.5 \text{ W}$ rated power
 - $U_{max2} = 350 \text{ V}$ maximum voltage
 - $\theta_{n2} = 70^\circ\text{C}$ rated temperature
 - $\theta_{max2} = 155^\circ\text{C}$ maximum temperature

- c) A carbon film resistor TA670, manufacturer Multicomp
 - $R_{n3} = 100000 \Omega$ rated resistance,
 - $P_{n3} = 1 \text{ W}$ rated power
 - $U_{max3} = 500 \text{ V}$ maximum voltage
 - $\theta_{n3} = 70^\circ\text{C}$ rated temperature
 - $\theta_{max3} = 155^\circ\text{C}$ maximum temperature

After the computations the critical resistances result for each type of resistor R_{crt1} , R_{crt2} , R_{crt3} .

- Plot $P_d(\theta)$ for each type of resistor
- Plot $U_a(\theta)$ for each type of resistor
- Define a maximum working temperature θ_{fmax} , for which the corresponding voltages will be computed. The initial value is $\theta_{fmax}=110$ degrees.

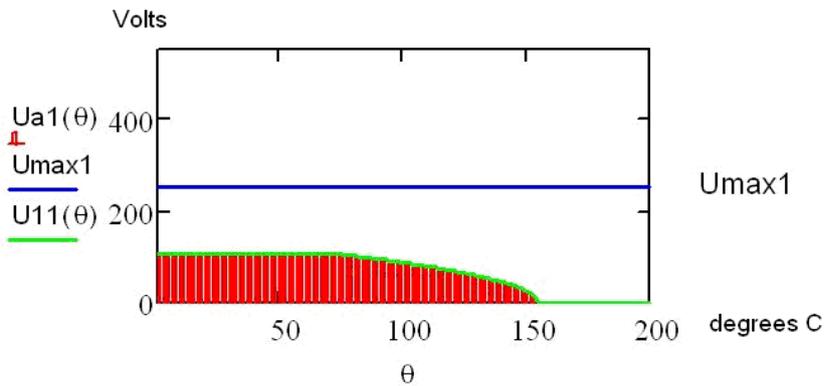

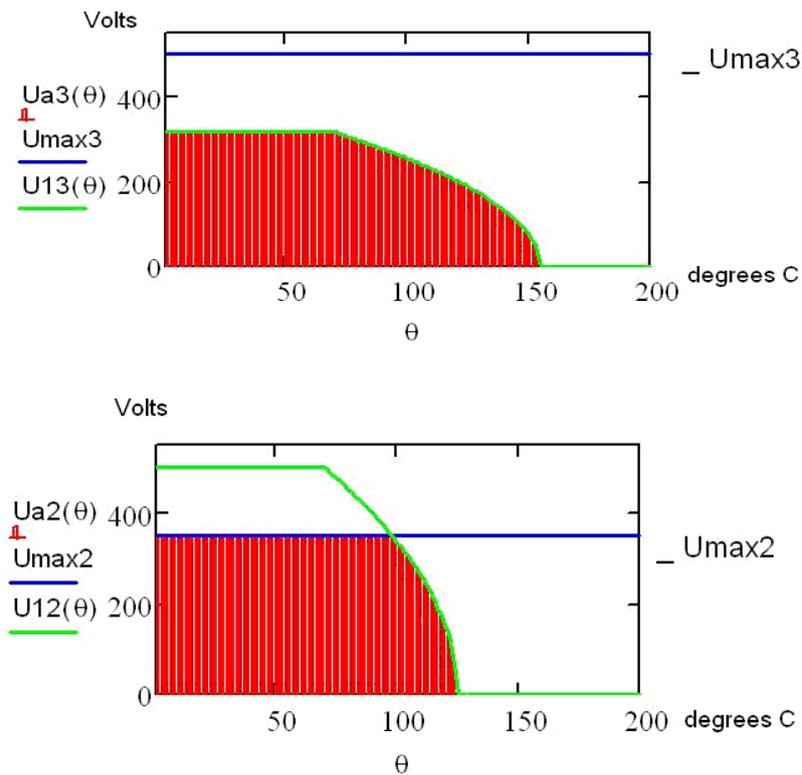


Fig. 3 The plots for the admissible voltage for the three resistors

The maximum admissible voltages result which can be applied for each type of resistor for an ambient temperature θ_{fmax} . The maximum admissible voltages will be mentioned for the following ambient temperatures θ_{fmax} : 20 degrees, 70 degrees, 100 degrees, 120 degrees by modifying the value in the program.

For the general case it will be used the plot that unites the individual stress for the three resistors $Ua1(\theta)$, $Ua2(\theta)$ and $Ua3(\theta)$. The admissible voltage results $U_{adm} = \min(Ua1(\theta_{fmax}), Ua2(\theta_{fmax}), Ua3(\theta_{fmax}))$

The electrical stress of a group of resistors will be mathematically defined in the paper for ranges of temperature. In this sense the temperature at the intersection points on the plots need to be determined.

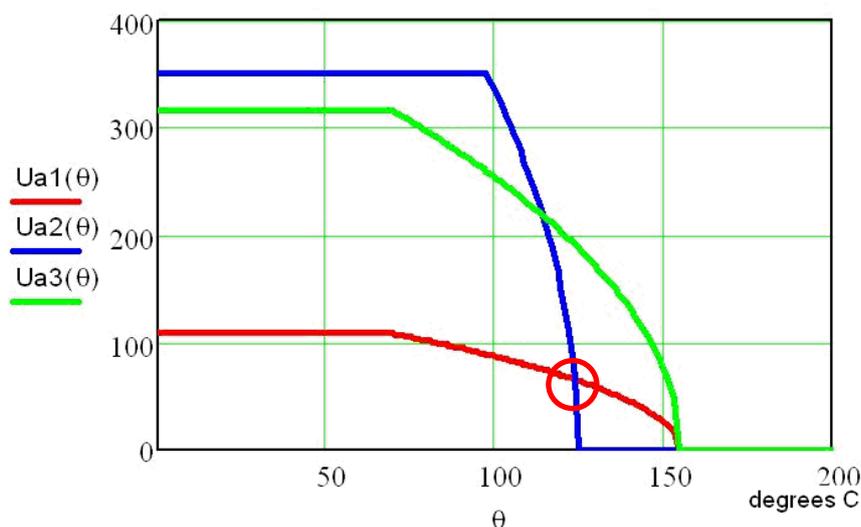


Fig 4. Plots for the power requirements of the three resistors

2.2 The same problem must be solved for other values of the rated resistance:

Carbon film resistor TA670	Carbon composition resistor CBT50	Carbon film resistor TA672
Rn1=360000 Ω	Rn2=390000 Ω	Rn3=75000 Ω

Homework (to be included in the paper): Solve the problem of electrical stress for a series of three resistors with the data given in section 2.1.

II. RESISTORS' FREQUENCY DEPENDENT BEHAVIOUR- COMPFREZ.XMCD -

COMPFREZ.XMCD is called.

Purpose: The study of the resistors' frequency dependent behaviour.

A cemented wire-wound resistor RBC 1003 is considered with the parameters:

R _n - 350 Ω	rated resistance
tol - 10 %	tolerance
P _n - 3 W	rated power

The wire-wound resistor was made as follows:

l _b - 14 mm	length of the wire-wounded part;
D _b - 3 mm	wire-wound diameter;
N - 28	number of turns.

The parasitic inductance is computed:

$$L_p = \frac{\mu N^2 S}{l}$$

The parasitic capacity is harder to compute and it is experimentally deduced: C_p>>0.3 pF.

Given this data the resonance frequency can be computed (formula [1] in Mathcad).

The plot in figure 5 allows quick estimation of the capacitive or inductive behavior of the resistor.

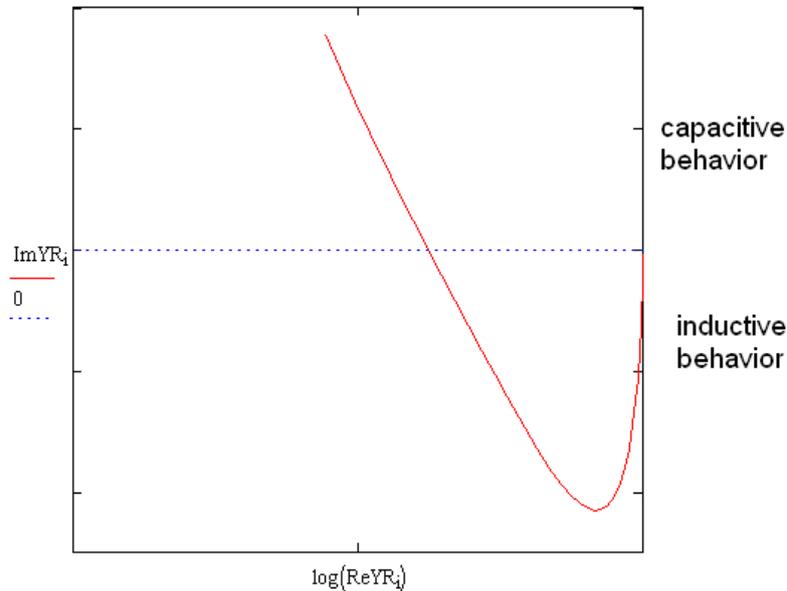


Fig. 5 Plotting the resistive, inductive or capacitive frequency dependent behaviour

For: $\omega = 0$ - purely resistive behavior
 $\omega \in (0, \omega_0)$ - inductive behavior
 $\omega > \omega_0$ - capacitive behavior

For values of resistance exceeding R_c (problem 3 in the annex) the resistor has only capacitive behavior.

From the theoretical model presented at the course, formula [3] allows us to compute the impedance of the considered resistor.

In figure 6 the variation $|Z|/R$ with respect to frequency is provided. The difference between f_o and f_r can be easily observed.

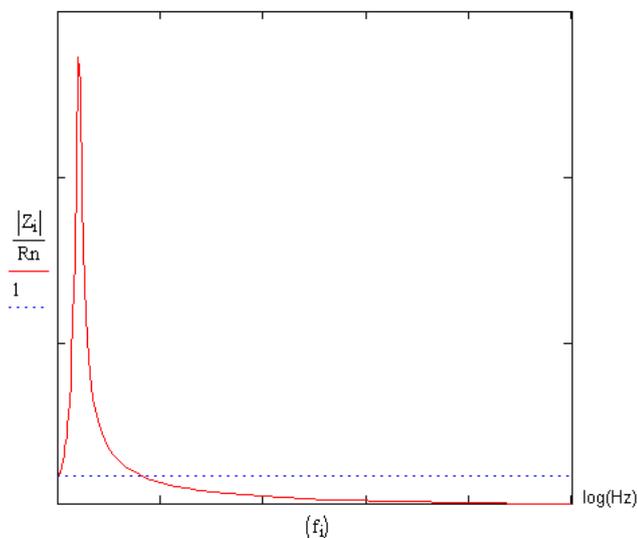


Fig. 6 The variation of the impedance's module within the frequency range

Homework: Solve problems [1, 2, 3 și 4] from Annex 5 = program COMPFREZ.XMCD.

III. CAPACITORS' FREQUENCY DEPENDENT BEHAVIOR COMPFCON.XMCD

COMPFCON.XMCD is called.

The program analyses the frequency dependent behavior of a capacitor, based on an equivalent circuit, through the study of the impedance $|Z(f)|$, and also the effect of connecting the capacitor in the circuit using two (inductive) traces.

The circuit used is given in the figure below:

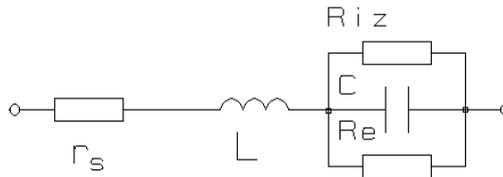


Fig. 7 The full series equivalent circuit of a capacitor.



Fig.8 Equivalent circuit of a capacitor

Where:

- r_s the resistance of the plates and of the terminals;
- L inductance of the plates and of the terminals;
- R_e dielectric loss resistance
- R_{iz} insulation resistance

The frequency dependence of C_s and $|Z(f)|$ is given below:

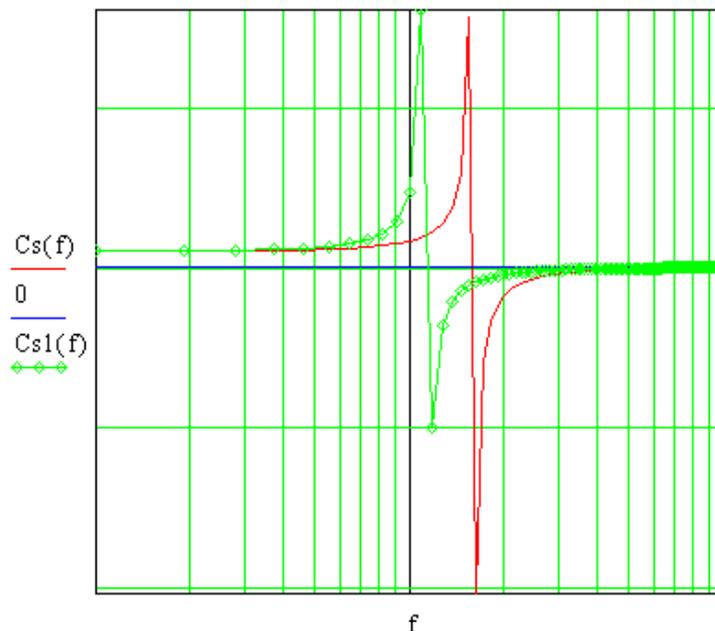


Fig. 9 The frequency dependence of C_s , the series equivalent capacity.

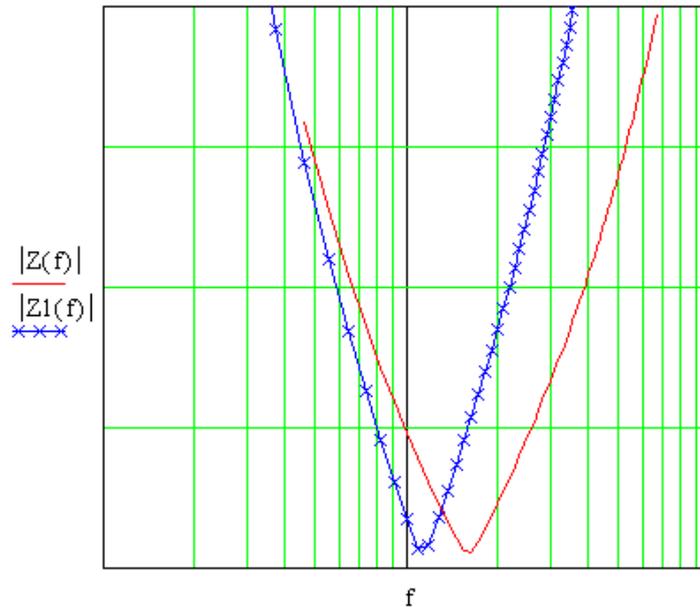


Fig 10 Impedance's modulus frequency dependence.

IV. THE ELECTRICAL STRESS OF THE CAPACITORS WITH FREQUENCY - SOLCON.XMCD-

SOLCON.XMCD is called.

SOLCON.XMCD shows how a capacitor is stressed with respect to frequency when a voltage is applied at its terminals. A short overview of the capacitors' parameters of interest to this paper is presented:

Rated capacitance, C – the capacitance inscribed on the body of the capacitor

Rated Voltage, U_n – maximum voltage that can be applied on the capacitor for a normal long term working regime.

Loss tangent, $\tan \delta$ - parameter which defines the active power losses in the capacitor, defined as the ratio between the active and reactive power ($\tan \delta = \frac{P_a}{P_r}$).

Rated power, P_n – maximum power that a capacitor can dissipate; power due to the dielectric losses.

Rated current, I_n – maximum current flowing through the capacitor. Its value is determined by the power losses between the capacitor's plates and terminals.

For a capacitor is provided the following data:

$$C = 68 \text{ nF},$$

$$U_n = 160 \text{ V},$$

$$P_n = 0.05 \text{ W},$$

$$I_n = 0,1 \text{ A},$$

$$\tan \delta = 8 \cdot 10^{-3}.$$

The frequency varies between (100, 100000) Hz with a 400 Hz step.

In accordance with the value of the maximum power dissipated by the capacitor P_{dmax} compared to the rated power there are the following cases:

- a) $P_n > P_{dmax}$,
- b) $P_n \leq P_{dmax}$

Correspondingly there are two different representations of the maximum voltage with respect to frequency (figures 11 and 12).

For case a) there are two characteristic frequencies for the capacitor f_α and f_β delimiting the stress ranges. For case b) there is only one characteristic frequency: f_c . The program chooses by taking into account P_{dmax} the corresponding proper case.

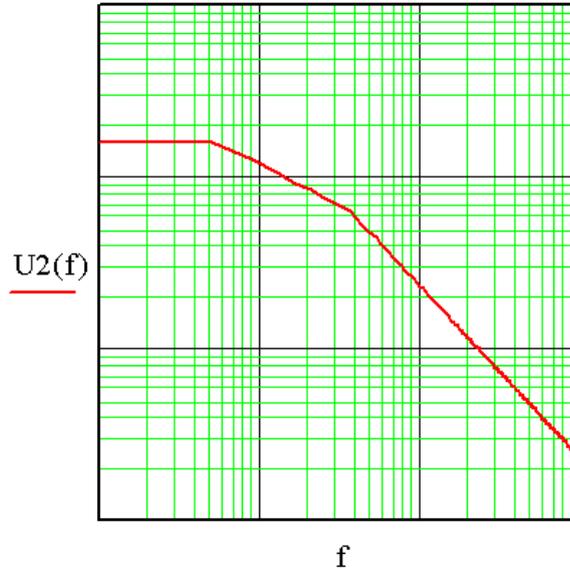


Fig. 11 Maximum voltage applied at the capacitor's terminals in the case $P_{dmax} > P_n$.

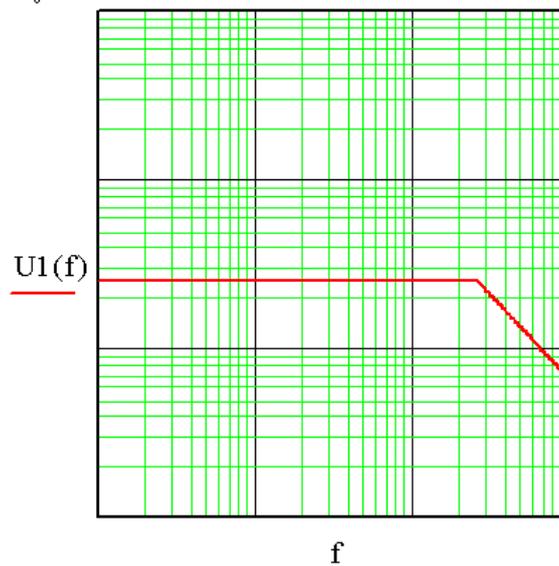


Fig. 12 Maximum voltage applied at the capacitor's terminals in the case $P_{dmax} < P_n$.

In case a), until the frequency f_α is reached the voltage must not be exceeded, hence the voltage U_n can be applied. At frequency f_α , due to the power dissipated in the dielectric, the rated power is reached and, from this frequency on, the voltage must correspondingly be decreased. At frequency f_β the rated current, I_n , is reached and, for even higher frequencies, the voltage must be further decreased.

The voltage formulas are:
 for $f < f_\alpha$ $U(f) = U_n$

$$\text{for } f_{\alpha} < f < f_{\beta} \quad U(f) = \sqrt{\frac{P_n}{2 \cdot \pi \cdot f \cdot C \cdot \text{tg } \delta}}$$

$$\text{for } f > f_{\beta} \quad U(f) = \frac{I_n}{2 \cdot \pi \cdot f \cdot C}$$

In case b) $P_{d\max} \leq P_n$, there is no power limitation because the value P_n is never reached, not even in the worst case scenario. When the frequency increases the rated current is reached at some point, value which must not be exceeded. The voltage is:

$$\text{for } f < f_c \quad U(f) = U_n$$

$$\text{for } f > f_c \quad U(f) = \frac{I_n}{2 \cdot \pi \cdot f \cdot C}$$